

Lab 5: Hands-On AC Analysis of NMOS  
Transistors  
EECS 170LB  
February 19, 2018

Roman Parise (59611417)  
Johnathan Fritsche (11106947)  
Jason Wang (42873192)

- 1 Introduction**
- 2 Procedure and Results - Voltage Transfer Curve**
- 3 Procedure and Results - Common Source Amplifier with Passive Load**
- 4 Conclusion**