

Lab 7  
EECS 170LB  
March 2, 2018

Roman Parise (59611417)  
Johnathan Fritsche (11106947)  
Jason Wang (42873192)

- 1 Introduction**
- 2 CMOS Inverter**
- 3 NAND and NOR Gate**
  - 3.1 NAND Gate**
  - 3.2 NOR Gate**
- 4 Conclusion**