

Lab 7
EECS 170LB
March 1, 2018

Roman Parise (59611417)
Johnathan Fritsche (11106947)
Jason Wang (42873192)

- 1 Introduction**
- 2 CMOS Inverter**
- 3 NAND and NOR Gate**
- 4 Conclusion**