

1 Common Source Amplifier

1.1 Procedure

The input source of the circuit in figure ?? is set to a $50mV_{pp}$ sinusoid with a $1kHz$ frequency. The sinusoidal input signal is offset by $2.5V$ DC, after making necessary adjustments to the bias point found in the previous portion of the experiment. The oscilloscope is set to measure time-domain signals to find the amplitude of the output signal. The gain of the amplifier is then calculated from the measurements and is compared to the theoretical result.

1.2 Results

The DC bias current I_D of the amplifier is found using the values found for V_{DD} , V_{out} , and R in the previous section.

$$I_D = \frac{V_{DD} - V_{out}}{R} = \frac{10V - 4.875V}{295.3\Omega} = 17.4mA \quad (1)$$

The theoretical transconductance g_m of the amplifier can be calculated using the given transconductance parameter k_n of $80mA/V$ and the I_D found in equation 1.

$$g_m = \sqrt{2k_n I_D} = \sqrt{2(80mA/V^2)(17.4mA)} = 52.8mA/V \quad (2)$$

The theoretical open loop gain A_{vo} of the amplifier can then be found using the transconductance g_m .

$$A_{vo} = -g_m R = -(52.8mA/V)(295.3\Omega) = -15.6V/V \quad (3)$$

$$gain \text{ in } dB = 20\log(|-15.6|) = 23.9dB \quad (4)$$

The following input and output voltages are measured using the oscilloscope.

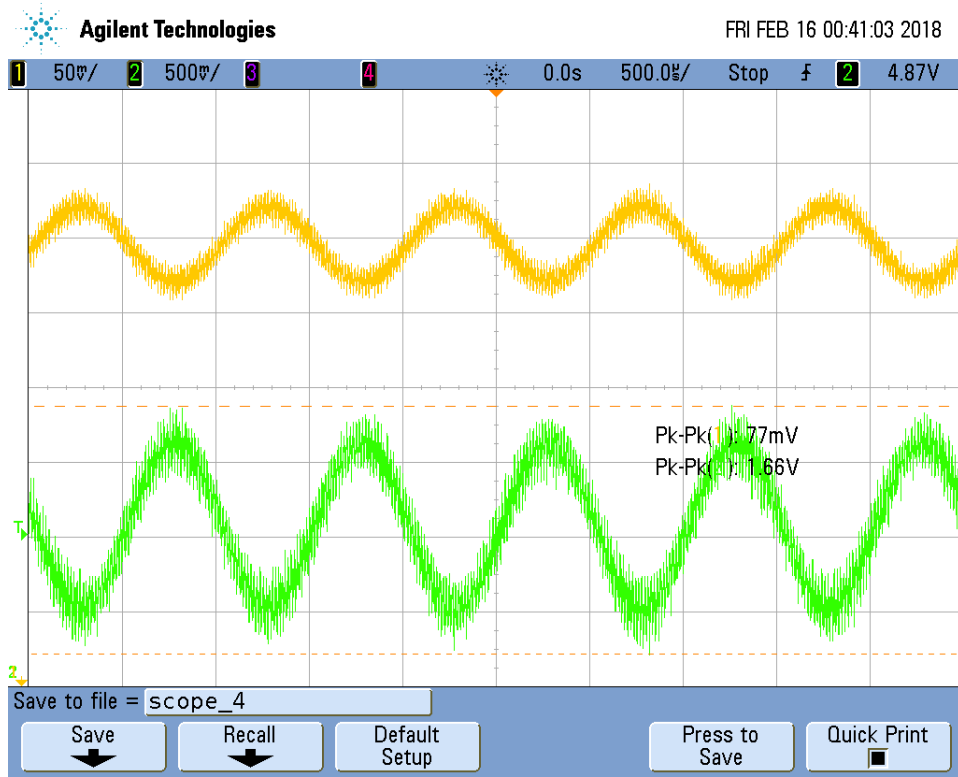


Figure 1: Input and Output Voltages Measured

From figure 1, the measured peak-to-peak amplitudes of V_{in} and V_{out} are $77mV_{pp}$ and $-1.66V_{pp}$, respectively. The peak-to-peak amplitude of the input signal measured from the oscilloscope will be used instead of the ideal $50mV_{pp}$ value set on the function generator because the signals measured on the oscilloscope account for noise, loading effects, and other nonidealities in the waveforms. The values found in figure 1 are used to calculate the measured gain of the amplifier.

$$A_{vo} = -\frac{V_{out}}{V_{in}} = \frac{-1.66V}{0.077V} = 21.6V/V \quad (5)$$

$$gain \text{ in } dB = 20\log(|-21.6|) = 26.7dB \quad (6)$$

The percent error of the measured and theoretical gains are found using the following equation:

$$error \text{ in amplitude gain} = -\left|\frac{(-21.6) - (-15.6)}{-15.6}\right| * 100\% = 38\% \quad (7)$$

$$error\ in\ dB\ gain = -|\frac{26.7dB - 23.9dB}{23.9dB}| * 100\% = 12\% \quad (8)$$

The measured gain and theoretical gain are in the same order of magnitude and the measured gain in dB is close to the theoretical value. Therefore, the measured results show that the theoretical model of the MOSFET is adequate in predicting experimental behavior.